
EE 671: VLSI Design Course

Brent Kung Adder Course Project

1. Without Delays

 

2. With gate-level Delays

